

PRE-WORK 2


2.2 PRELIMINARY WORK

2.2.2 2-TO-1 MULTIPLEXER


Condensed truth table:

S	F
0	A[3:0]
1	B[3:0]


The schematic:

 

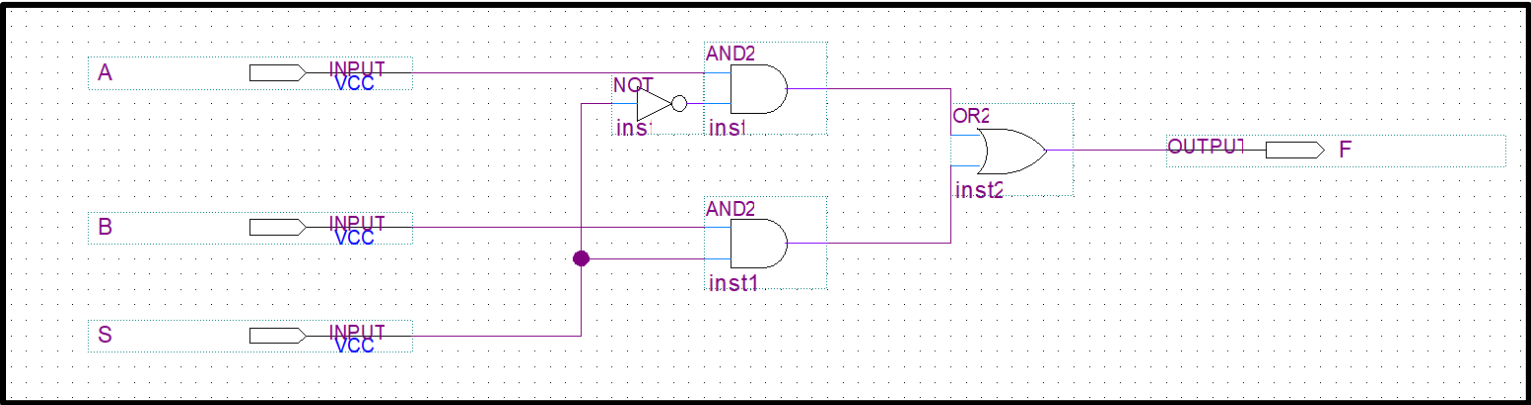The schematic representation in 1-bit (MUX):



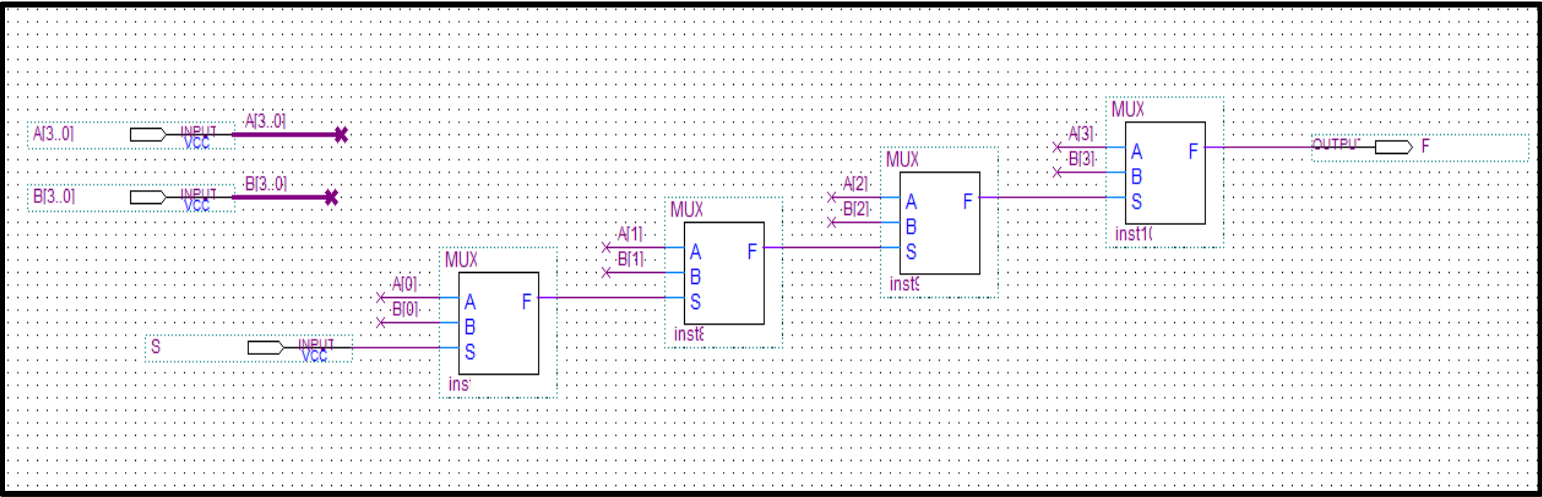After converting to a symbol (in 4-bit) (multiplexer):




### Verilog code (in procedural format):

```
module multiplexer(A, B, S, F);  
    parameter size = 4;  
    input [size-1:0] A, B;  
    input S;  
    output F;  
    wire [size-2:0] w;  
    genvar i;  
    generate  
    for (i=0 ; i<size; i=i+1) begin: multiplexer  
        if(i==0)  
            MUX U1(A[i], B[i], S, w[i]);  
        else if (i==size-1)  
            MUX U1(A[i], B[i], w[i-1], F);  
        else  
            MUX U1(A[i], B[i], w[i-1], w[i]);  
        end  
    endgenerate  
endmodule
```
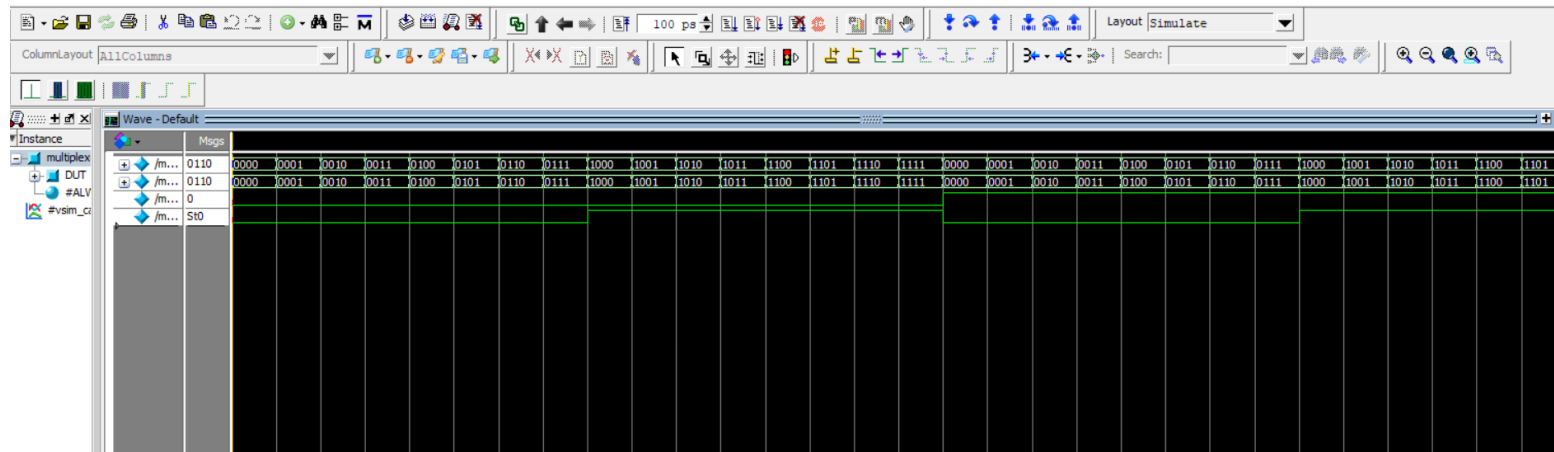
### And Verilog Code For the MUX :

```
module MUX(A, B, S, F);  
    input A, B, S;  
    output F;  
    wire w1, w2;  
    and G1(w1, A, !S);  
    and G2(w2, B, S);  
    or G3(F, w1, w2);  
endmodule
```



The simulation of the multiplexer in Modelsim

### 2.2.3 4-BIT ADDER/SUBTRACTOR

1)

Cin	A	B	Cout	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{SUM} = \text{Cin} \oplus A \oplus B$$

$$\text{Cout} = (\text{Cin}' + B')(\text{Cin}' + A')(A' + B') = A.B + \text{Cin}(A \oplus B)$$

2)

Verilog code to implement the full adder:

```


module add_sub_circuit(A, B, Cin, Cout, SUM);
    input A, B, Cin;
    output Cout, SUM;
    wire w1, w2, w3;

    xor G1(w1, A, B);
    and G2(w2, A, B);
    and G3(w3, Cin, w1);
    xor G4(SUM, w1, Cin);
    or G5(Cout, w2, w3);
endmodule


```

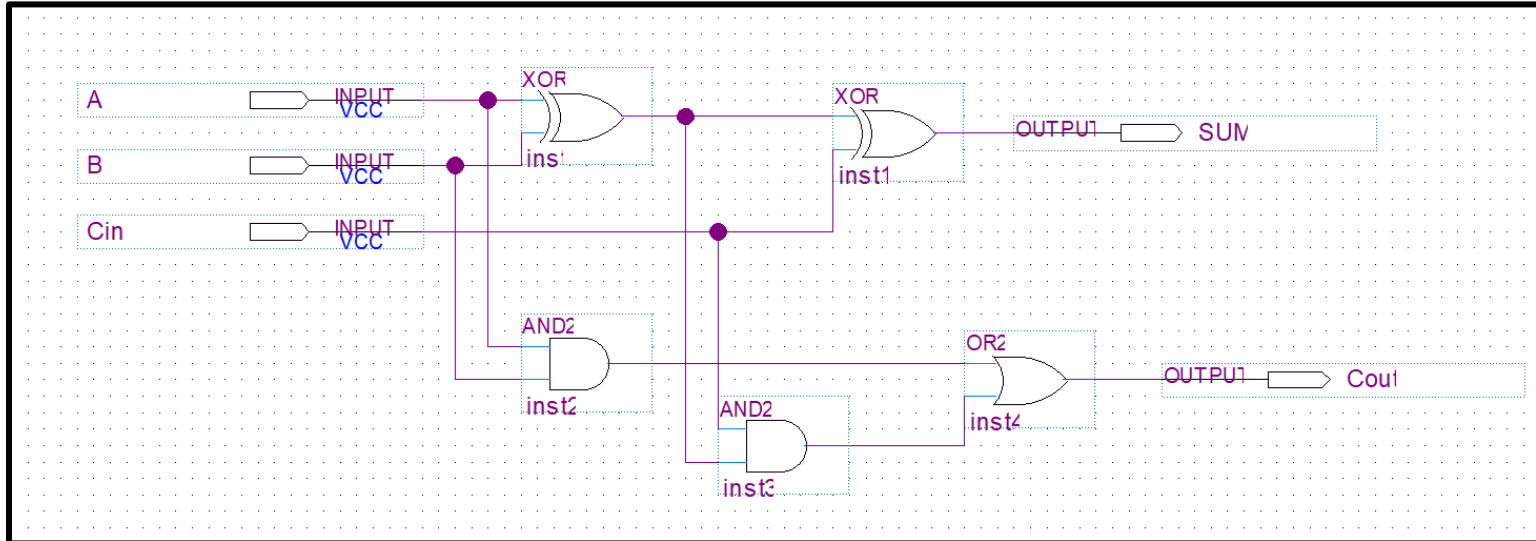3)

The schematic for the full adder in 1-bit:



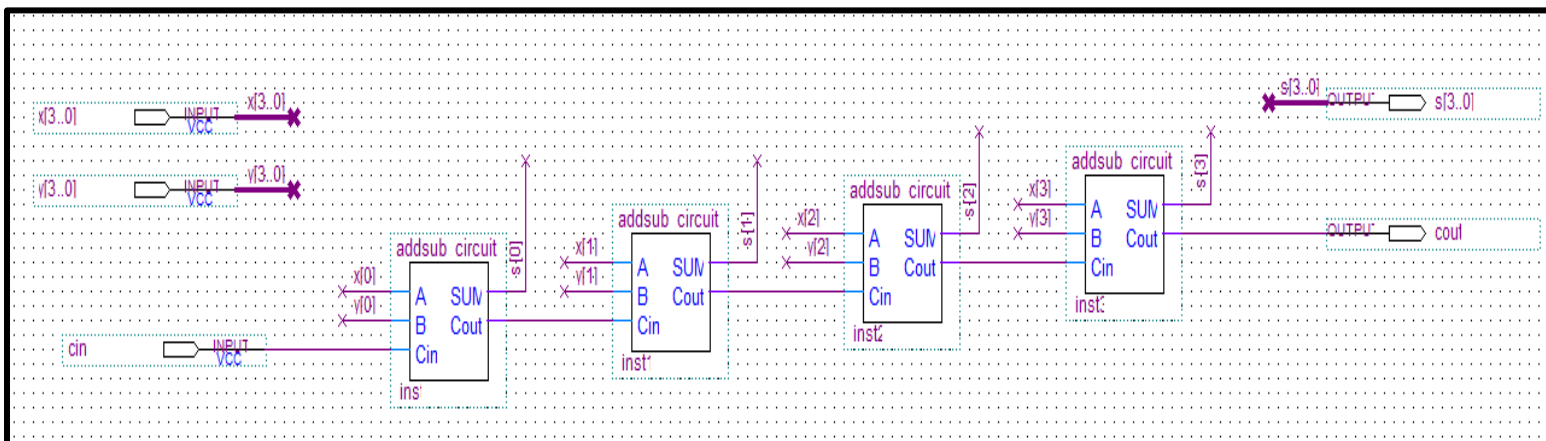The schematic representation of 4-bit Ripple-Carry-Adder:



4)

Verilog code to implement 4-bit Ripple-Carry-Adder:

```
module add_sub (x, y, cin, cout, s);
```

```
    parameter size = 4 ;
```

```
    input [size-1:0] x, y;
```

```
    input cin;
```

```
    output [size-1:0] s;
```

```
    output cout;
```

```
    wire [size-2:0] w;
```

```
    genvar i;
```

```
generate
for (i=0 ; i<size; i=i+1) begin:add_sub
if (i==0)
    add_sub_circuit U1(x[i], y[i], cin, s[i], w[i]);
else if(i==size-1)
    add_sub_circuit U1(x[i], y[i], w[i-1], s[i], cout);
else
    add_sub_circuit U1(x[i], y[i], w[i-1], s[i], w[i]);
end
endgenerate
endmodule
```


5)

OP	A	B	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

After simplifying from the K-map;  **$F = A + B + OP$**

7)

 **Modelsim simulation for the first adder/subtractor circuit (with Cin):**



### Verilog code for the new circuit (with OP-for the symbol):

```
module OP_signal(B, OP, F);
    input B, OP;
    output F;
    wire w1, w2;

    and (w1, B, !OP);
    and (w2, !B, OP);
    or (F, w1, w2);

endmodule
```

### Verilog code for the new circuit (with OP):

```
module add_sub_OP (A, B, OP, cout, s);
    parameter size = 4 ;

    input [size-1:0] A, B;
    input OP;
    output [size-1:0] s;
    output cout;
    wire [size-1:0] w;

    genvar i;
    generate
    for (i=0 ; i<size; i=i+1) begin:add_sub_OP
        if (i==0) begin
            OP_signal U2(B, OP, w[i]);
            add_sub_circuit U1(A[i], w[i], OP, s[i], w[i+1]);
        end
        else if(i==size-1)
            add_sub_circuit U1(A[i], w[i], OP, s[i], cout);
        else
            add_sub_circuit U1(A[i], w[i], OP, s[i], w[i+1]);
        end
    endgenerate
endmodule
```

## Testbench for the new circuit with all possibilities:

```
module add_sub_OP_tb();
    parameter size = 4;
    reg [size-1:0] A, B;
    reg OP;
    wire [size-1:0] s;
    wire cout;

    add_sub_OP DUT (A, B, OP, cout, s);

    always
    begin
        A=4'b0000; B=4'b0000; OP=1'b0; #100;
        A=4'b0001; B=4'b0001; OP=1'b0; #100;
        A=4'b0010; B=4'b0010; OP=1'b0; #100;
        A=4'b0011; B=4'b0011; OP=1'b0; #100;
        A=4'b0100; B=4'b0100; OP=1'b0; #100;
        A=4'b0101; B=4'b0101; OP=1'b0; #100;
        A=4'b0110; B=4'b0110; OP=1'b0; #100;
        A=4'b0111; B=4'b0111; OP=1'b0; #100;
        A=4'b1000; B=4'b1000; OP=1'b0; #100;
        A=4'b1001; B=4'b1001; OP=1'b0; #100;
        A=4'b1010; B=4'b1010; OP=1'b0; #100;
        A=4'b1011; B=4'b1011; OP=1'b0; #100;
        A=4'b1100; B=4'b1100; OP=1'b0; #100;
        A=4'b1101; B=4'b1101; OP=1'b0; #100;
        A=4'b1110; B=4'b1110; OP=1'b0; #100;
        A=4'b1111; B=4'b1111; OP=1'b0; #100;


        A=4'b0000; B=4'b0000; OP=1'b0; #100;
        A=4'b0001; B=4'b0001; OP=1'b0; #100;
        A=4'b0010; B=4'b0010; OP=1'b0; #100;
        A=4'b0011; B=4'b0011; OP=1'b0; #100;
        A=4'b0100; B=4'b0100; OP=1'b0; #100;
        A=4'b0101; B=4'b0101; OP=1'b0; #100;
        A=4'b0110; B=4'b0110; OP=1'b0; #100;
        A=4'b0111; B=4'b0111; OP=1'b0; #100;
        A=4'b1000; B=4'b1000; OP=1'b0; #100;
        A=4'b1001; B=4'b1001; OP=1'b0; #100;
        A=4'b1010; B=4'b1010; OP=1'b0; #100;
```

```

A=4'b1011; B=4'b1011; OP=1'b0; #100;
A=4'b1100; B=4'b1100; OP=1'b0; #100;
A=4'b1101; B=4'b1101; OP=1'b0; #100;
A=4'b1110; B=4'b1110; OP=1'b0; #100;
A=4'b1111; B=4'b1111; OP=1'b0; #100;
end
endmodule

```

 The simulation for the new circuit (with OP):



## 2.2.4 4-BIT COMPARATOR

1)

The truth table:


A1	A0	B1	B0	A<B	A>B	A=B
0	0	0	0	0	0	1
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	1	0
0	1	0	1	0	0	1
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	0




1	0	1	0	0	0	1
1	0	1	1	1	0	0
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	0	0	1

### K-Maps:

For the output  $F1 = A < B$ :

 

For  $F2 = A > B$ :

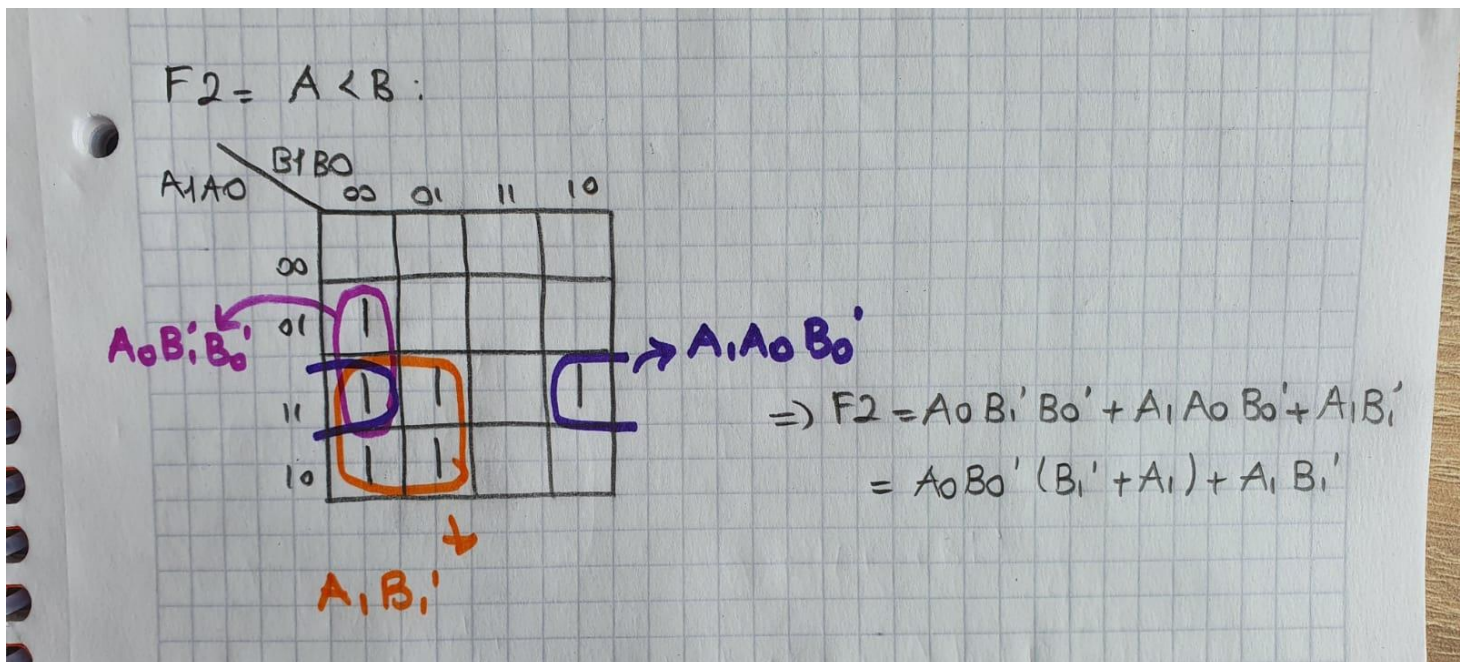

For  $F3 = A=B$ :

$F3 = A=B$ :

$A1A0 \backslash B1B0$	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1

$$\begin{aligned}
 F3 &= A1'A0'B1'B0' + A1'A0B1'B0 + A1A0B1B0 + A1A0'B1B0' \\
 &= A0'B0'(A1'B1' + A1B1) + A0B0(A1'B1' + A1B1) \\
 &= (A1'B1' + A1B1)(A0'B0' + A0B0) \\
 &= (A1 \oplus B1)'(A0 \oplus B0)'
 \end{aligned}$$

2)

```

module comparator(A, B, F1, F2, F3);
    parameter size = 4;
    input [size-1:0] A, B;
    output F1, F2, F3;
    wire w1, w2, w3, w4, w5, w6;

    or (F1, w1, w4);
    or (F2, w2, w5);
    or (F3, w3, w6);

    genvar i;
    generate
    for (i=0 ; i<size ; i=i+1) begin: comparator
        if (i==0 || i==1)
            comparator_circuit U1(A[i], B[i], w4, w5, w6);
        else
            comparator_circuit U1(A[i], B[i], w1, w2, w3);
        end
    endgenerate

```

```
endmodule
```

**3)**

```
module comparator_tb();
```

```
    parameter size = 4;
```

```
    reg [size-1:0] A, B;
```

```
    wire F1, F2, F3;
```

```
    comparator DUT(A, B, F1, F2, F3);
```

```
    always
```

```
    begin
```

```
        A=4'b0000; B=4'b0000; #100;
```

```
        A=4'b0000; B=4'b0001; #100;
```

```
        A=4'b0000; B=4'b0010; #100;
```

```
        A=4'b0000; B=4'b0011; #100;
```

```
        A=4'b0000; B=4'b0100; #100;
```

```
        A=4'b0000; B=4'b0101; #100;
```

```
        A=4'b0000; B=4'b0110; #100;
```

```
        A=4'b0000; B=4'b0111; #100;
```

```
        A=4'b0000; B=4'b1000; #100;
```

```
        A=4'b0000; B=4'b1001; #100;
```

```
        A=4'b0000; B=4'b1010; #100;
```

```
        A=4'b0000; B=4'b1011; #100;
```

```
        A=4'b0000; B=4'b1100; #100;
```

```
        A=4'b0000; B=4'b1101; #100;
```

```
        A=4'b0000; B=4'b1110; #100;
```

```
        A=4'b0000; B=4'b1111; #100;
```

```
        A=4'b0001; B=4'b0000; #100;
```

```
        A=4'b0001; B=4'b0001; #100;
```

```
        A=4'b0001; B=4'b0010; #100;
```

```
        A=4'b0001; B=4'b0011; #100;
```

```
        A=4'b0001; B=4'b0100; #100;
```

```
        A=4'b0001; B=4'b0101; #100;
```

```
        A=4'b0001; B=4'b0110; #100;
```

```
        A=4'b0001; B=4'b0111; #100;
```

```
        A=4'b0001; B=4'b1000; #100;
```

```
        A=4'b0001; B=4'b1001; #100;
```

```
        A=4'b0001; B=4'b1010; #100;
```

```
        A=4'b0001; B=4'b1011; #100;
```

A=4'b0001; B=4'b1100; #100;  
A=4'b0001; B=4'b1101; #100;  
A=4'b0001; B=4'b1110; #100;  
A=4'b0001; B=4'b1111; #100;

A=4'b0010; B=4'b0000; #100;  
A=4'b0010; B=4'b0001; #100;  
A=4'b0010; B=4'b0010; #100;  
A=4'b0010; B=4'b0011; #100;  
A=4'b0010; B=4'b0100; #100;  
A=4'b0010; B=4'b0101; #100;  
A=4'b0010; B=4'b0110; #100;  
A=4'b0010; B=4'b0111; #100;  
A=4'b0010; B=4'b1000; #100;  
A=4'b0010; B=4'b1001; #100;  
A=4'b0010; B=4'b1010; #100;  
A=4'b0010; B=4'b1011; #100;  
A=4'b0010; B=4'b1100; #100;  
A=4'b0010; B=4'b1101; #100;  
A=4'b0010; B=4'b1110; #100;  
A=4'b0010; B=4'b1111; #100;

A=4'b0011; B=4'b0000; #100;  
A=4'b0011; B=4'b0001; #100;  
A=4'b0011; B=4'b0010; #100;  
A=4'b0011; B=4'b0011; #100;  
A=4'b0011; B=4'b0100; #100;  
A=4'b0011; B=4'b0101; #100;  
A=4'b0011; B=4'b0110; #100;  
A=4'b0011; B=4'b0111; #100;  
A=4'b0011; B=4'b1000; #100;  
A=4'b0011; B=4'b1001; #100;  
A=4'b0011; B=4'b1010; #100;  
A=4'b0011; B=4'b1011; #100;  
A=4'b0011; B=4'b1100; #100;  
A=4'b0011; B=4'b1101; #100;  
A=4'b0011; B=4'b1110; #100;  
A=4'b0011; B=4'b1111; #100;

A=4'b0101; B=4'b0000; #100;  
A=4'b0101; B=4'b0001; #100;

A=4'b0101; B=4'b0010; #100;  
A=4'b0101; B=4'b0011; #100;  
A=4'b0101; B=4'b0100; #100;  
A=4'b0101; B=4'b0101; #100;  
A=4'b0101; B=4'b0110; #100;  
A=4'b0101; B=4'b0111; #100;  
A=4'b0101; B=4'b1000; #100;  
A=4'b0101; B=4'b1001; #100;  
A=4'b0101; B=4'b1010; #100;  
A=4'b0101; B=4'b1011; #100;  
A=4'b0101; B=4'b1100; #100;  
A=4'b0101; B=4'b1101; #100;  
A=4'b0101; B=4'b1110; #100;  
A=4'b0101; B=4'b1111; #100;

A=4'b0111; B=4'b0000; #100;  
A=4'b0111; B=4'b0001; #100;  
A=4'b0111; B=4'b0010; #100;  
A=4'b0111; B=4'b0011; #100;  
A=4'b0111; B=4'b0100; #100;  
A=4'b0111; B=4'b0101; #100;  
A=4'b0111; B=4'b0110; #100;  
A=4'b0111; B=4'b0111; #100;  
A=4'b0111; B=4'b1000; #100;  
A=4'b0111; B=4'b1001; #100;  
A=4'b0111; B=4'b1010; #100;  
A=4'b0111; B=4'b1011; #100;  
A=4'b0111; B=4'b1100; #100;  
A=4'b0111; B=4'b1101; #100;  
A=4'b0111; B=4'b1110; #100;  
A=4'b0111; B=4'b1111; #100;

A=4'b1000; B=4'b0000; #100;  
A=4'b1000; B=4'b0001; #100;  
A=4'b1000; B=4'b0010; #100;  
A=4'b1000; B=4'b0011; #100;  
A=4'b1000; B=4'b0100; #100;  
A=4'b1000; B=4'b0101; #100;  
A=4'b1000; B=4'b0110; #100;  
A=4'b1000; B=4'b0111; #100;  
A=4'b1000; B=4'b1000; #100;

```

A=4'b1000; B=4'b1001; #100;
A=4'b1000; B=4'b1010; #100;
A=4'b1000; B=4'b1011; #100;
A=4'b1000; B=4'b1100; #100;
A=4'b1000; B=4'b1101; #100;
A=4'b1000; B=4'b1110; #100;
A=4'b1000; B=4'b1111; #100;

```

```

A=4'b1001; B=4'b0000; #100;
A=4'b1001; B=4'b0001; #100;
A=4'b1001; B=4'b0010; #100;
A=4'b1001; B=4'b0011; #100;
A=4'b1001; B=4'b0100; #100;
A=4'b1001; B=4'b0101; #100;
A=4'b1001; B=4'b0110; #100;
A=4'b1001; B=4'b0111; #100;
A=4'b1001; B=4'b1000; #100;
A=4'b1001; B=4'b1001; #100;
A=4'b1001; B=4'b1010; #100;
A=4'b1001; B=4'b1011; #100;
A=4'b1001; B=4'b1100; #100;
A=4'b1001; B=4'b1101; #100;
A=4'b1001; B=4'b1110; #100;
A=4'b1001; B=4'b1111; #100;

```

```

end
endmodule

```

### Modelsim simulation of the comparator



## 2.2.6 DECODER

### The Verilog code:

```
module decoder (num, left_out, right_out);
    input [3:0] num;
    output [7:0] left_out, right_out;
    reg [7:0] left_out, right_out;

    always @(num)
    case (num)
        4'b0000 : right_out = 8'b00000001;
        4'b0001 : right_out = 8'b01100000;
        4'b0010 : right_out = 8'b11011010;
        4'b0011 : right_out = 8'b11110010;
        4'b0100 : right_out = 8'b01100110;
        4'b0101 : right_out = 8'b10110100;
        4'b0110 : right_out = 8'b10111110;
        4'b0111 : right_out = 8'b11100000;
        4'b1000 : right_out = 8'b01100000;
        4'b1001 : right_out = 8'b11011010;
        4'b1010 : right_out = 8'b11110010;
        4'b1011 : right_out = 8'b01100110;
        4'b1100 : right_out = 8'b10110100;
        4'b1101 : right_out = 8'b10111110;
        4'b1110 : right_out = 8'b11100000;
        4'b1111 : right_out = 8'b11111110;

        4'b0000 : left_out = 8'b00000000;
        4'b0001 : left_out = 8'b00000000;
        4'b0010 : left_out = 8'b00000000;
        4'b0011 : left_out = 8'b00000000;
        4'b0100 : left_out = 8'b00000000;
        4'b0101 : left_out = 8'b00000000;
        4'b0110 : left_out = 8'b00000000;
        4'b0111 : left_out = 8'b00000000;
        4'b1000 : left_out = 8'b00000010;
        4'b1001 : left_out = 8'b00000010;
        4'b1010 : left_out = 8'b00000010;
        4'b1011 : left_out = 8'b00000010;
        4'b1100 : left_out = 8'b00000010;
```

```
4'b1101 : left_out = 8'b00000010;  
4'b1110 : left_out = 8'b00000010;  
4'b1111 : left_out = 8'b00000010;
```

```
endcase  
endmodule
```